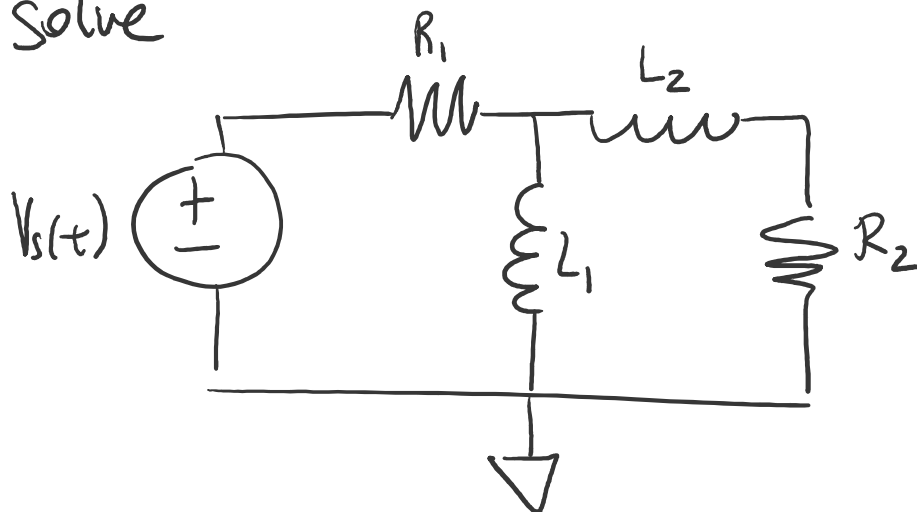



18220 Exam 2 xTRA PRACTICE

1st circuit?

Solve




CCCIRCUIT?

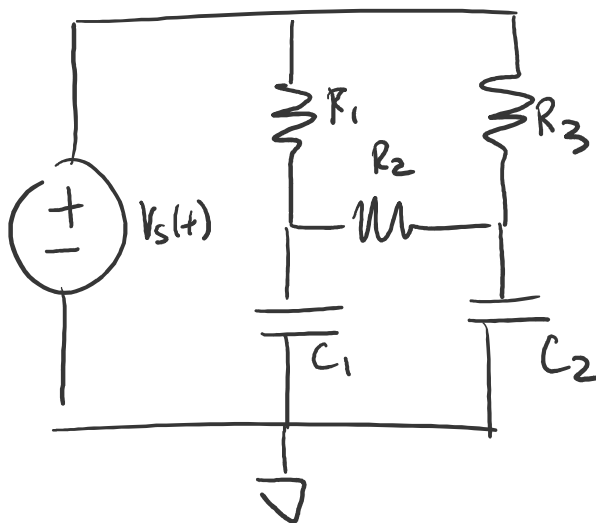





WHICH REFERENCE?

lots of you guys were confused about ref. dir. so...

consider the following junction

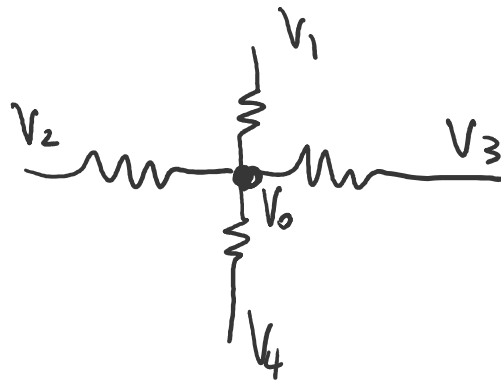

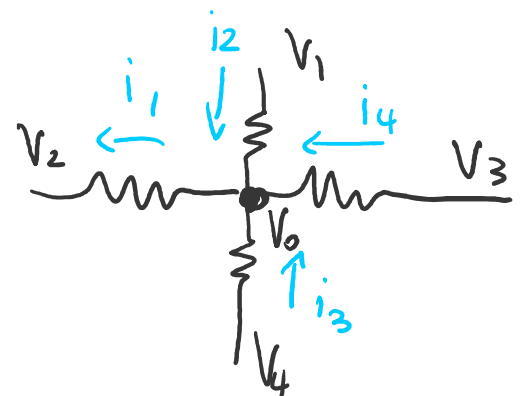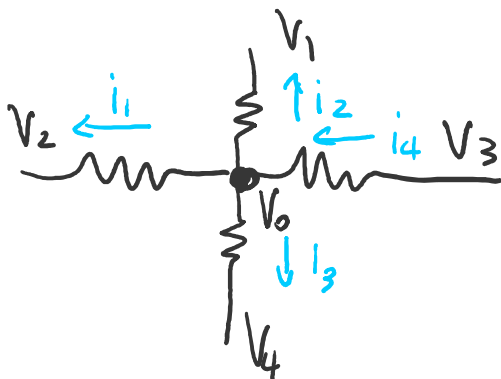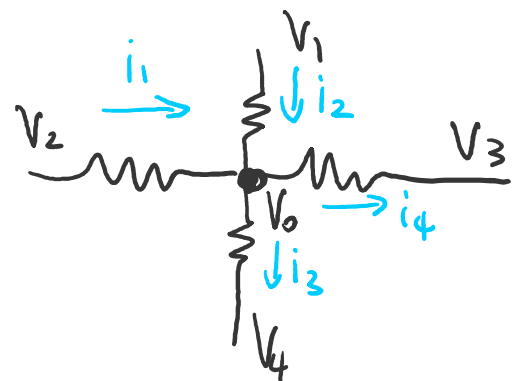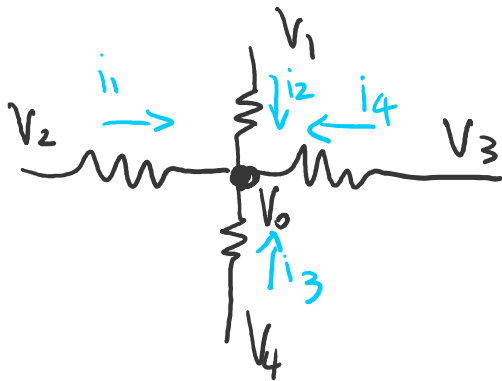Use KCL to write an equation for the junction w/
the following conventions:



Hopefully you observe something...